Circuit diagram:

- 20 V source (with $+$ over $-$) on the left
- Current i flowing through a $1.2\,\text{k}\Omega$ resistor with voltage $+\,V_1\,-$ across it
- Dependent source $V_0 = 3V_1$ (diamond, marked $-\;+$)
- $2\,\text{k}\Omega$ resistor with voltage $+\,V_2\,-$ across it